


From Transistors to Computers


On voltage and current

Metaphor: Electricity is air.


- **Voltage:** pressure. Wants to flow from high pressure to low pressure.
- **Current:** flow. The amount of (air, charge) going past
- **Resistance:** narrow tube. Restricts the amount of flow that can go through.

Transistors ("n-FET")

 


 

Making a NOT gate

 


Making a NAND gate

 

Transistors ("p-FET")

When the **G**ate has
sufficiently **lower**
voltage than the
Source

Note the source is
at the top now.

 


Current
can flow
this way

The bubble is the
difference in the diagram.




BOBA FET



Making a NOT gate better using CMOS

 

Making a NAND gate better using CMOS


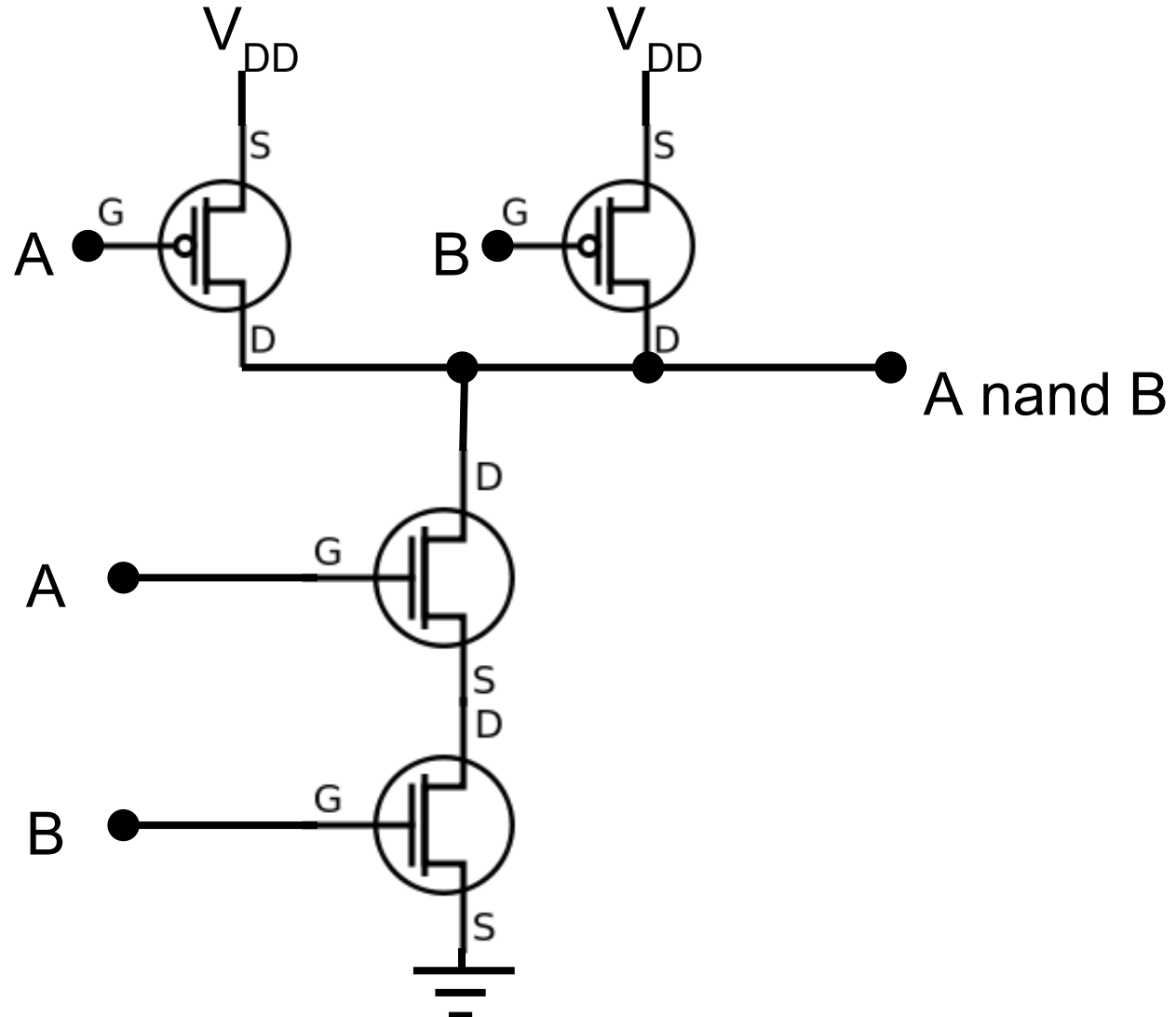


  You can build logic gates out of other logic gates.




Some useful pieces



Decoder

  

Multiplexer

 


Full Adder

  


Square Wave Source




Arithmetic Logic Unit

 







Arithmetic Logic Unit

 

Latch

 

Register

      

Register



Instructions!

Structure of an instruction



16 bits wide

Structure of an instruction



Opcodes

- Some to do math
 - **ADD** - $A + B$
 - **AND** - bitwise A and B
 - **OR** - bitwise A or B
 - **XOR** - bitwise A xor B
 - **NEG** - negative A
 - **SHL** - shift A left by 1 bit
 - **SHR** - shift A right by 1 bit
 - **INV** - bitwise invert A

Opcodes

- Some interact with RAM
 - **LD** - load address A from RAM
 - **STO** - store B to RAM at address A
- Some manage flow control
 - **JNZ** - jump to B if A not zero
 - **JZ** - jump to B if A zero

Opcodes to Binary!

- **ADD** - 0000
- **AND** - 0001
- **OR** - 0010
- **XOR** - 0011
- **NEG** - 0100
- **SHL** - 0101
- **SHR** - 0110
- **INV** - 0111
- **??** - 1000
- **??** - 1001
- **??** - 1010
- **??** - 1011
- **LD** - 1100
- **STO** - 1101
- **JZ** - 1110
- **JNZ** - 1111


Memory in our computer

- 2^{16} bytes of RAM (64 kilobytes)
- 16 registers (scratch space)
- Register 0 is always 0. Writes to it do nothing.

Structure of an instruction



Structure of an instruction

 

Opcodes to Binary!

- **ADD** - 0000
- **AND** - 0001
- **OR** - 0010
- **XOR** - 0011
- **NEG** - 0100
- **SHL** - 0101
- **SHR** - 0110
- **INV** - 0111
- **ADDI** - 1000
- **ANDI** - 1001
- **ORI** - 1010
- **XORI** - 1011
- **LD** - 1100
- **STO** - 1101
- **JZ** - 1110
- **JNZ** - 1111


**We're ready to build our
computer!**

Plan: 3 Phases


- **Fetch:** Get the current instruction from memory
- **Decode:** Make the calculations based on the current instruction
- **Execute:** Actually store the results, and calculate the location of the next instruction

All these phases are managed by the ticking of square waves (not shown in the upcoming slides: imagine them)

Fetch Phase

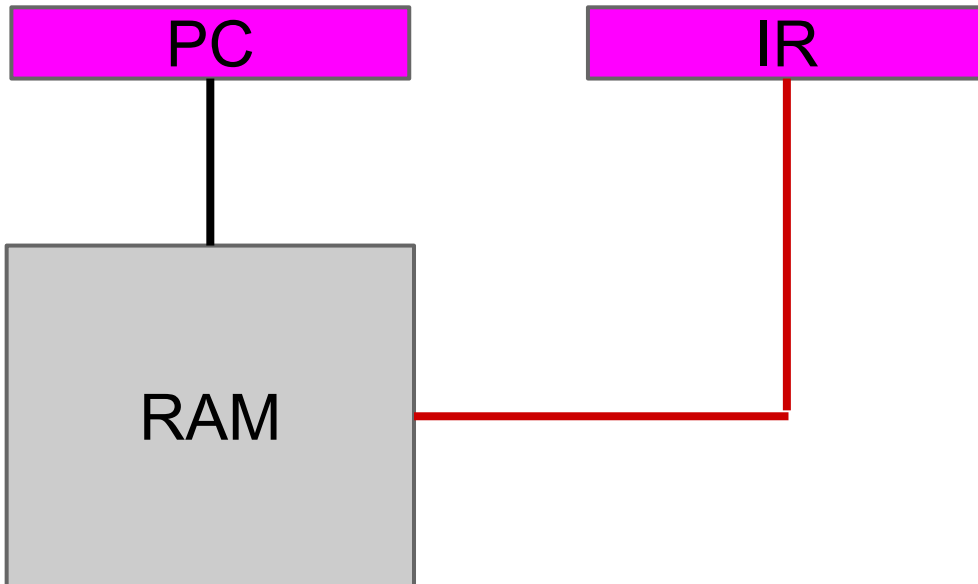

Decode phase

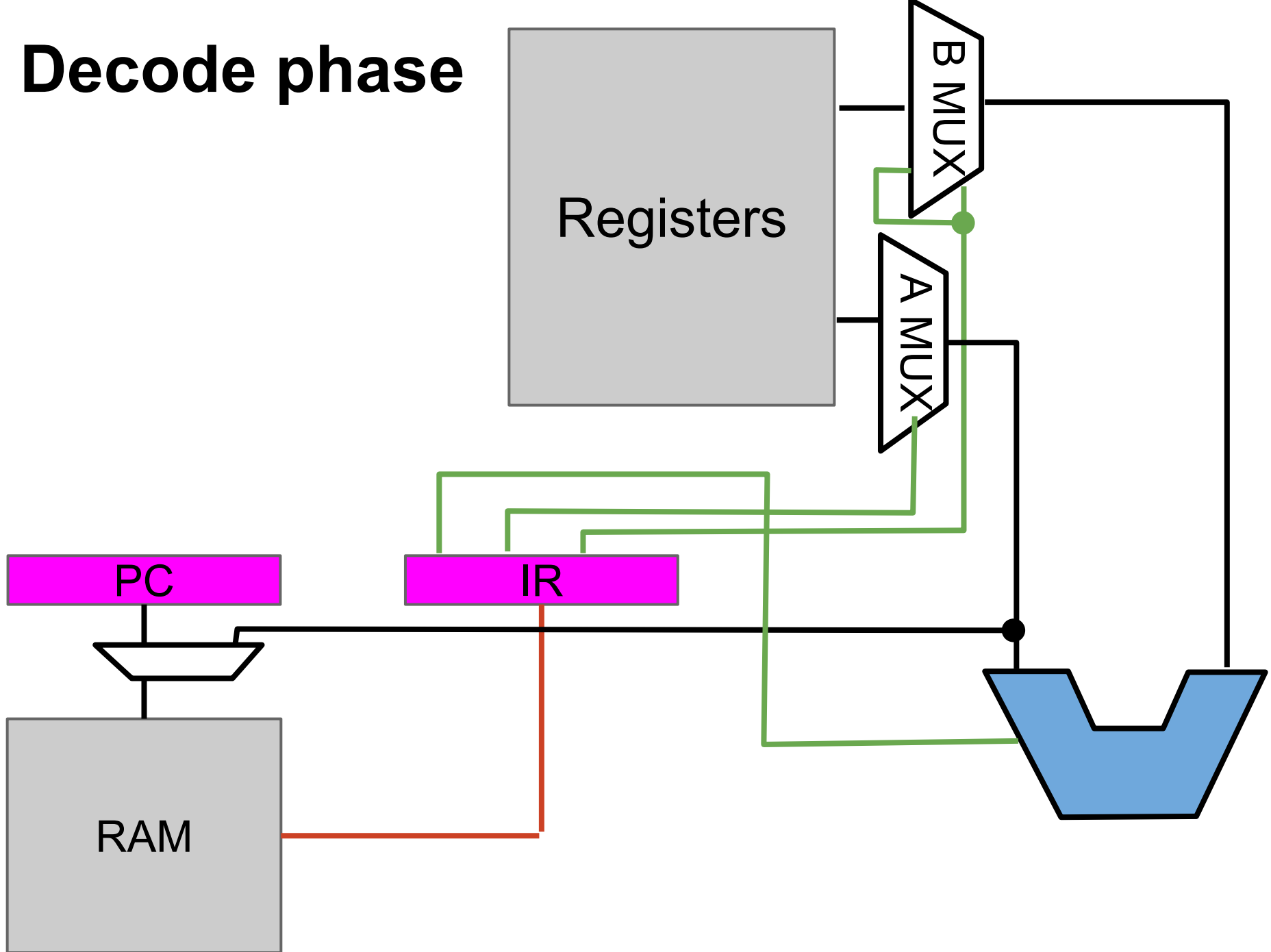

Execute phase

